


 **ganeshprabhu2005** / **ENCODER8TO3DATAFLOW** Public







forked from [naavaneetha/ENCODER8TO3DATAFLOW](#)

 GPL-3.0 license

 **0 stars**  **331 forks**  **Branches**  **Tags**  **Activity**

 **Star**

 **Notifications**

 **Code**  **Pull requests**  **Actions**  **Projects**  **Security**  **Insights**

main

1 Branch

0 Tags

Go to file

Go to file

Code

This branch is [1 commit ahead of naavaneetha/ENCODER8TO3DATAFLOW:main](#) .

ganeshprabhu2005 Update README.md

2 weeks ago

	db	EXP5	3 months ago
	incremental_db	EXP5	3 months ago
	output_files	EXP5	3 months ago
	simulation/modelsim	EXP5	3 months ago
	ENCODER8TO3.qpf	EXP5	3 months ago
	ENCODER8TO3.qsf	EXP5	3 months ago
	ENCODER8TO3.qws	EXP5	3 months ago
	ENCODER8TO3.v	EXP5	3 months ago
	ENCODER8TO3.v.bak	EXP5	3 months ago
	LICENSE	Initial commit	3 months ago
	README.md	Update README.md	2 weeks ago
	Waveform.vwf	EXP5	3 months ago

README
 License

ENCODER 8TO3 DATAFLOW Modelling

AIM:

To implement Encoder 8 To 3 in Dataflow Modelling using verilog and validating their functionality using their functional tables

SOFTWARE REQUIRED: Quartus prime

THEORY

Encoder 8 To 3

The 8 to 3 line Encoder is also known as Octal to Binary Encoder. In 8 to 3 line encoder, there is a

total of eight inputs, i.e., D₀, D₁, D₂, D₃, D₄, D₅, D₆, and D₇ and three outputs, i.e., A₀, A₁, and A₂. In 8-input lines, one input-line is set to true at a time to get the respective binary code in the output side. Below are the block diagram and the truth table of the 8 to 3 line encoder.

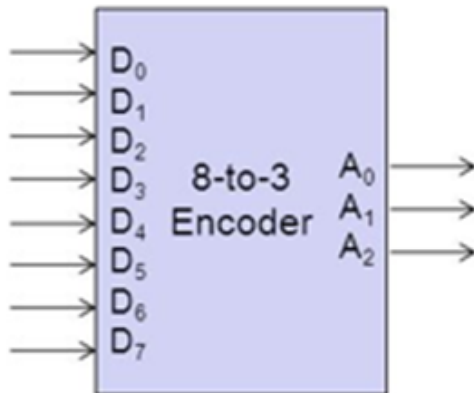


Figure 01 Block Diagram of Encoder 8 * 3

Truth Table

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

The logical expression of the term A₀, A₁, and A₂ are as follows:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

Logical circuit of the above expressions is given below:



 


Figure 02 Encoder 8 * 3

Procedure

- 1.Type the program in Quartus software.
- 2.Compile and run the program.
- 3.Generate the RTL schematic and save the logic diagram.
- 4.Create nodes for inputs and outputs to generate the timing diagram.
- 5.For different input combinations generate the timing diagram.



/* write all the steps invloved */

PROGRAM


/* Program for Encoder 8 To 3 in Dataflow Modelling and verify its truth table in quartus using Verilog programming.


Developed by: GANESH PRABHU J RegisterNumber: 212223220023

```
/* Program for Encoder 8 To 3 in Dataflow Modelling and verify its truth table in
quartus using Verilog programming.
module encoder_top(din, a, b, c);
input [0:7] din;
output a,b,c;
assign a=din[4] | din[5] | din[6] | din[7];
assign b=din[2] | din[3] | din[6] | din[7];
assign c=din[2] | din[4] | din[6] | din[7];
endmodule
```




 RTL LOGIC FOR Encoder 8 To 3 in Dataflow Modelling



 

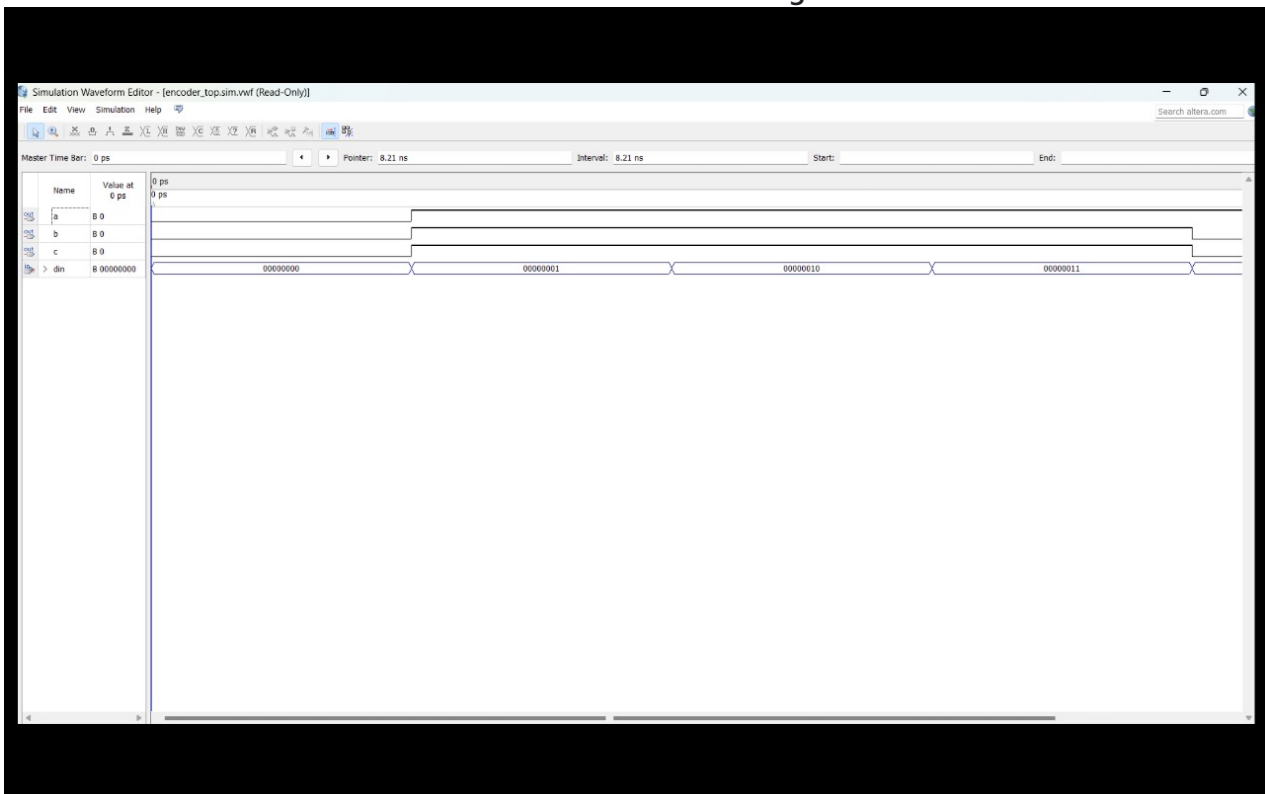TIMING DIGRAMS FOR Encoder 8 To 3 in Dataflow Modelling



RESULTS

Releases

No releases published

Packages

No packages published

Languages

● HTML 65.6% ● Verilog 28.5% ● Standard ML 5.9%